## SOFT CIRCUITS

E-Textiles Workshop
 Fabricademy Bootcamp
 2025
 Rebekka Jochem

Disclaimer: This presentation was created for educational purposes as part of the fabricademy bootcamp 2025. While many of the images and diagrams are my own, some photographs and visual materials included are the property of their respective copyright holders. Please do not share, reproduce, or distribute this presentation without my permission. If you are a rights holder and would like an image removed, please contact me directly. Thank you for your understanding.

#### WELCOME!

Introduction

What are E-Textiles?

- Soft Electronics 101

Practical Experimentation

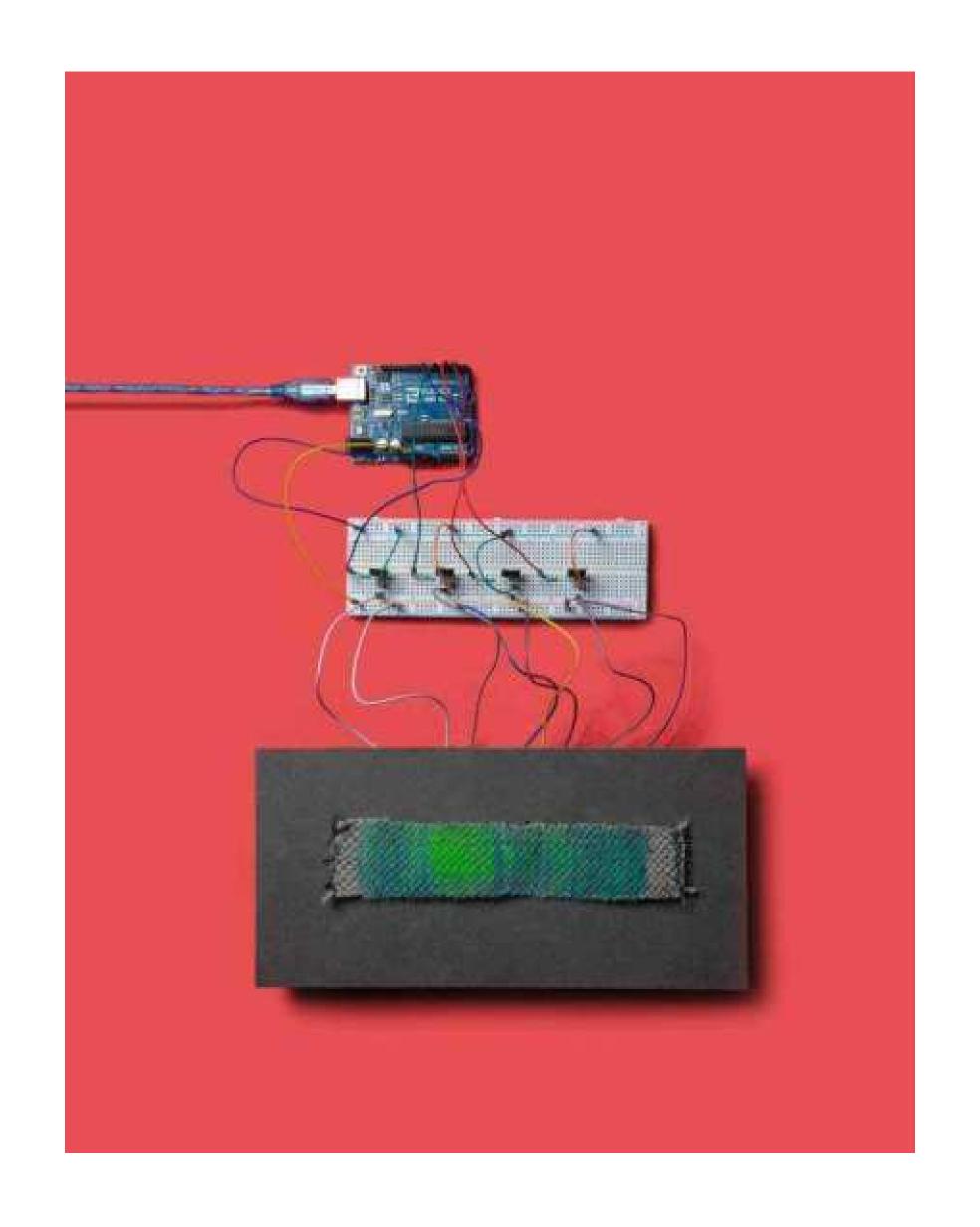




Figure 1



Figure 2

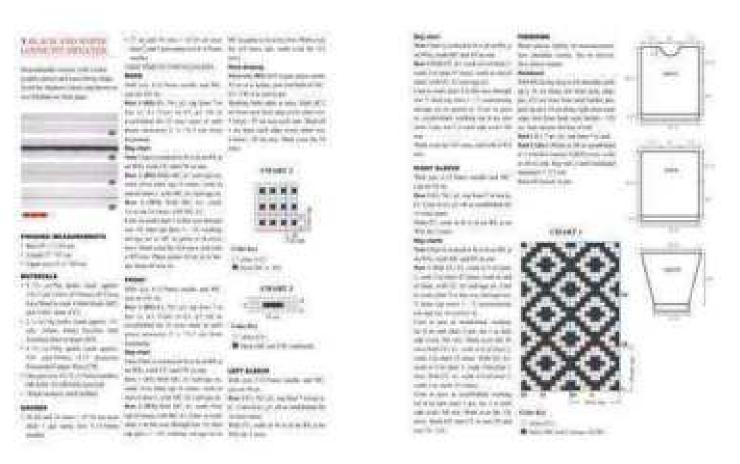



Figure 3

Figure 1: Article published 1967 in the Cosmopolitan Magazine, advertising computer programming as a promising career for young women.

Figure 2: Image from an advertisment for Fairchild Semiconductors (1969), framing the assembly of electronics in their factory as the modern extension of indigenous crafts and reproductive labor.

Figure 3: The knitting instructions for Irene Posch's and Ebru Kurbak's Knitted Radio, which is a fully textile FM Transmitter that can also be worn as a sweater.

Sources: Figure 1, Figure 2, Figure 3.

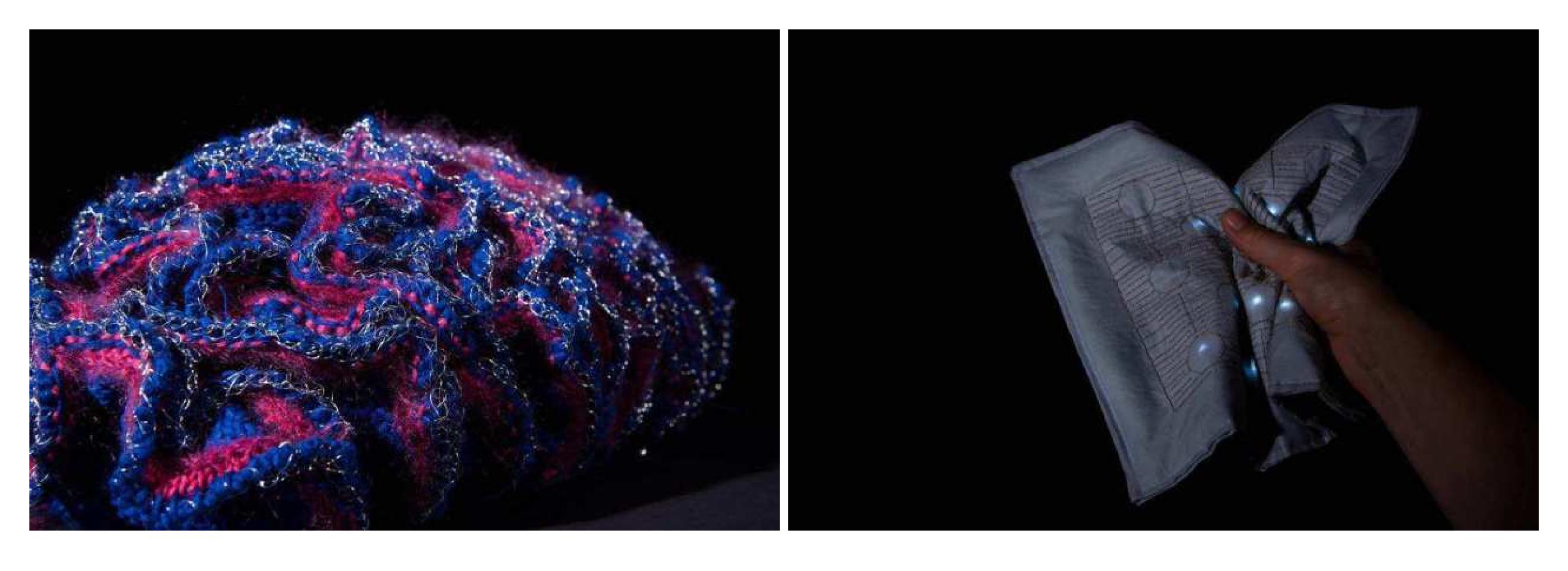



#### → Snapchat





Travescripe London Central Aldgate Fast

<sup>↗</sup> Google Maps



Period Tracker




#### Make choices that are right for you

Learn about your body from the data in your app and our science-based articles to make informed health choices.


→ Clue



<sup>▶</sup> Flo Health

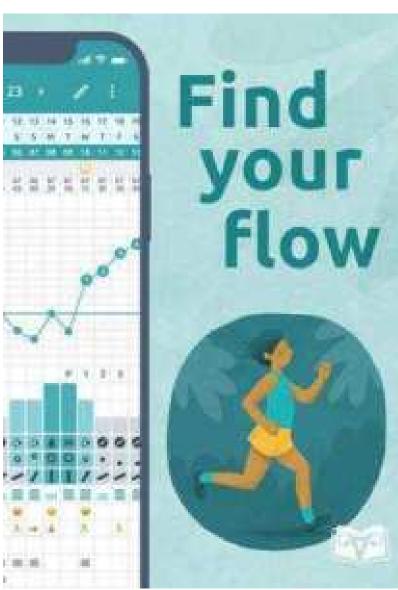

<sup>→</sup> Read your body

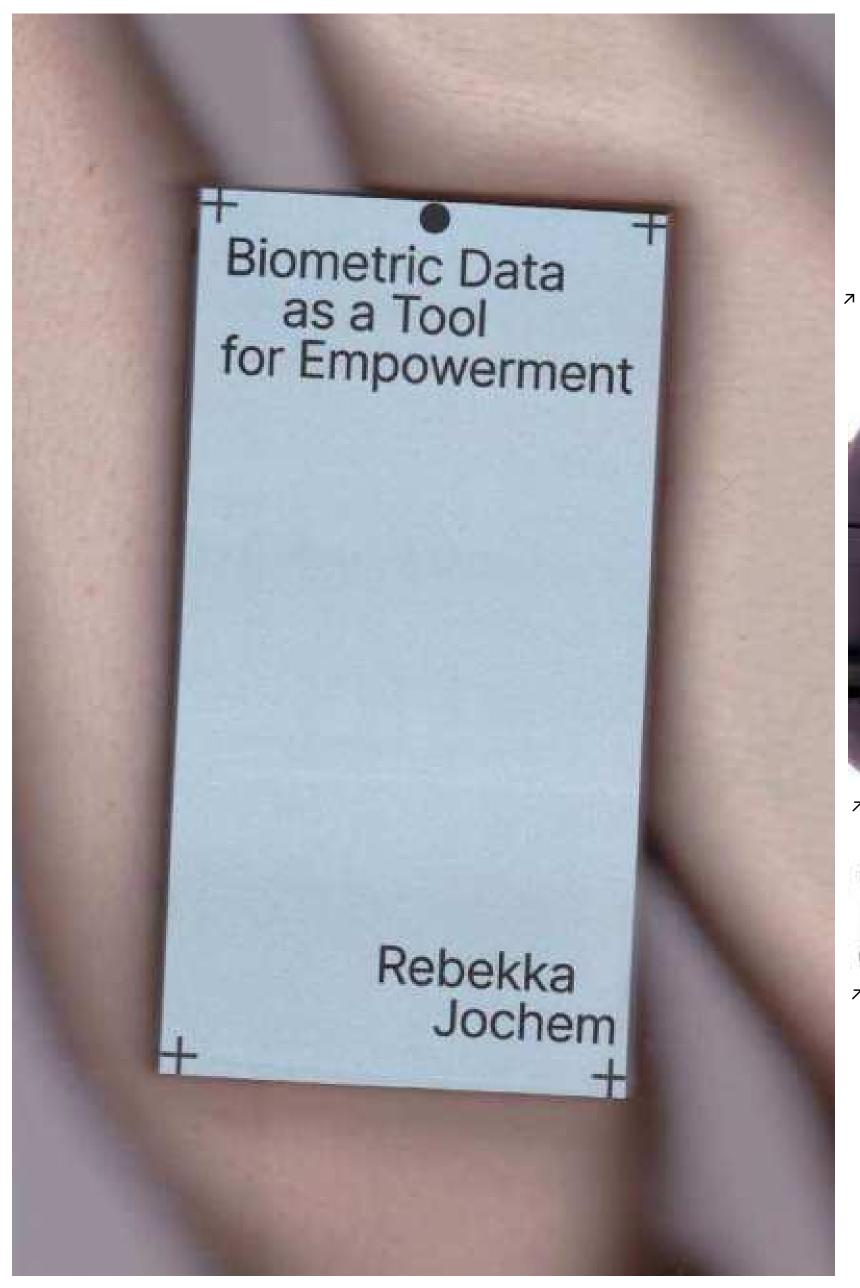






Garrini



→ Perfect365




→ Bellabeat

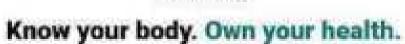

Distributed the soon




→ Strava

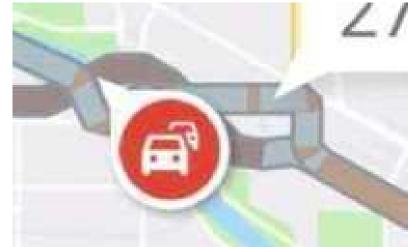


<sup>↗</sup> Google Maps



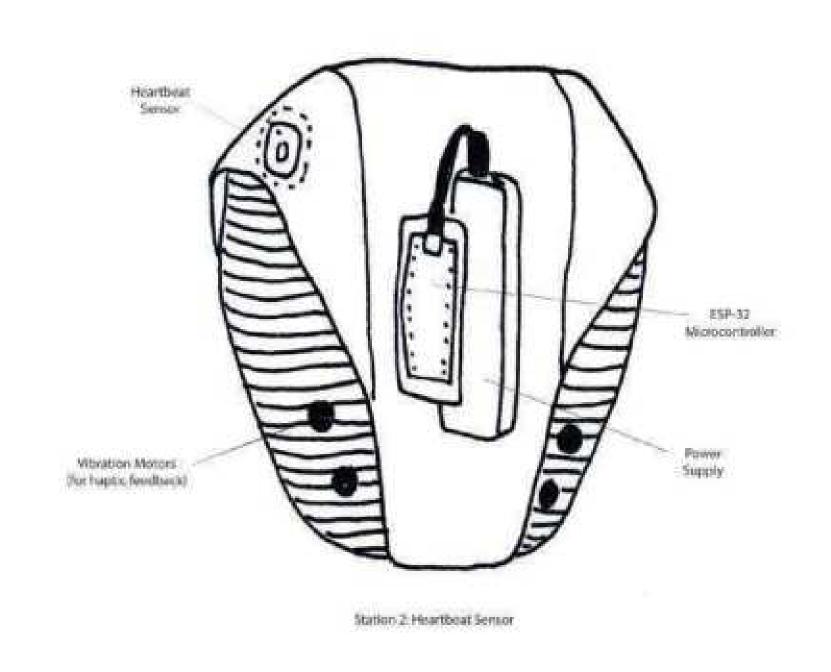



You+/Rebekka Jochem/2024

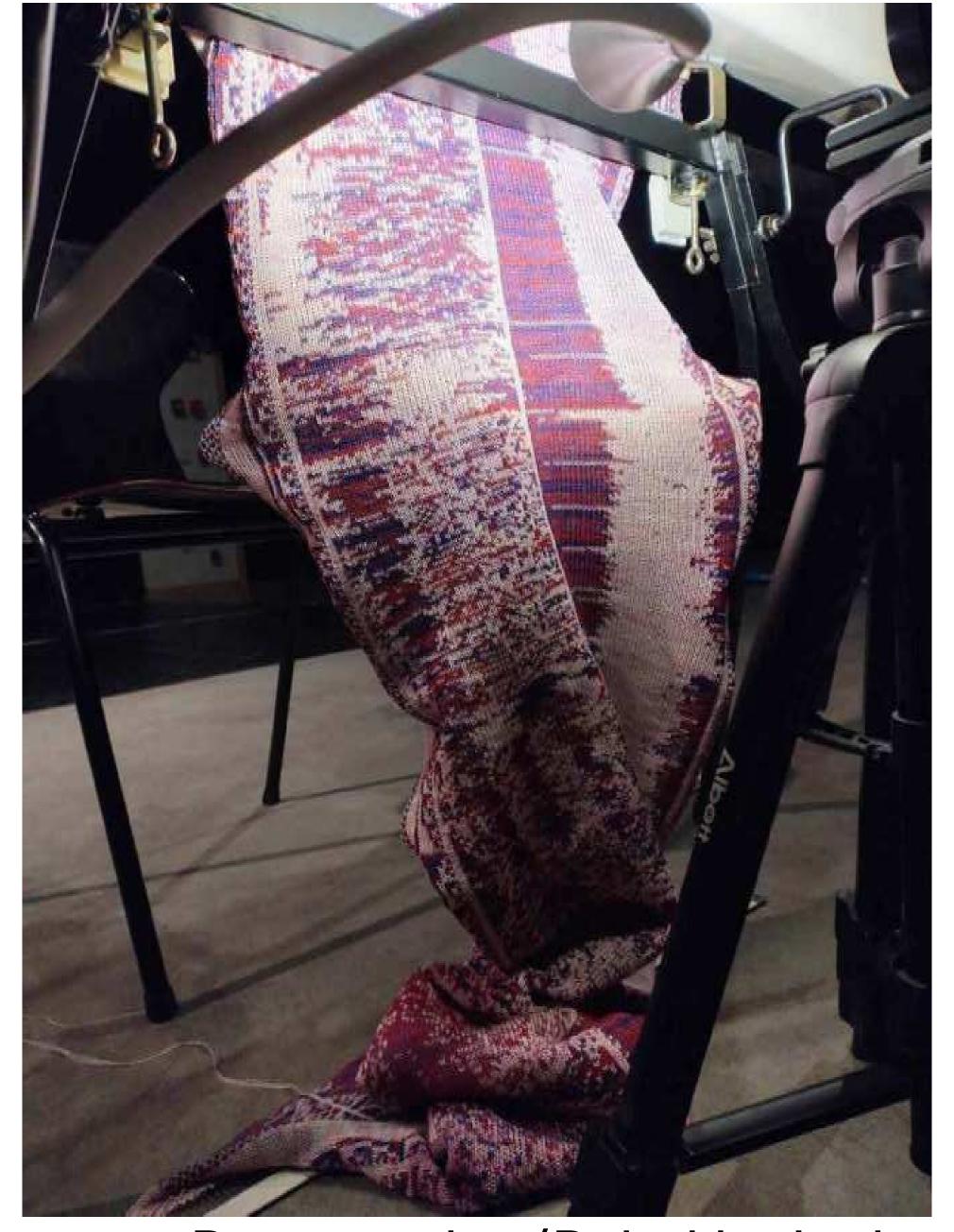

Repatterning/Rebekka Jochem & Agnetha Jaunich/2025

#### WHAT ARE E-TEXTLES?

#### SPACE TRAVEL



I-Suit Spacesuit Gloves / ILC Dover Inc. & SOFTSWITCH Ltd. / 2001


#### FITNESS TRACKING





### FILM LIGHTING



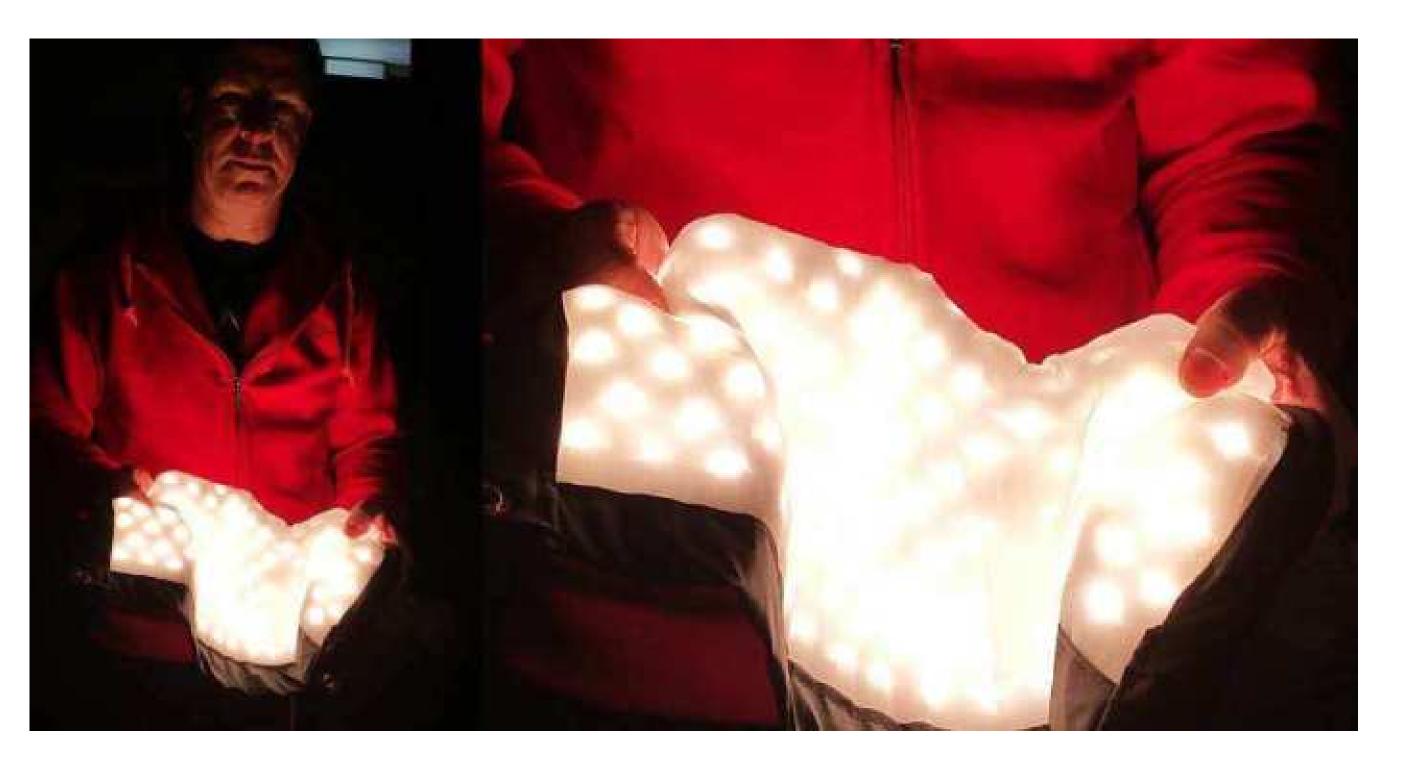



### EDUCATION






#### INTERACTION DESIGN

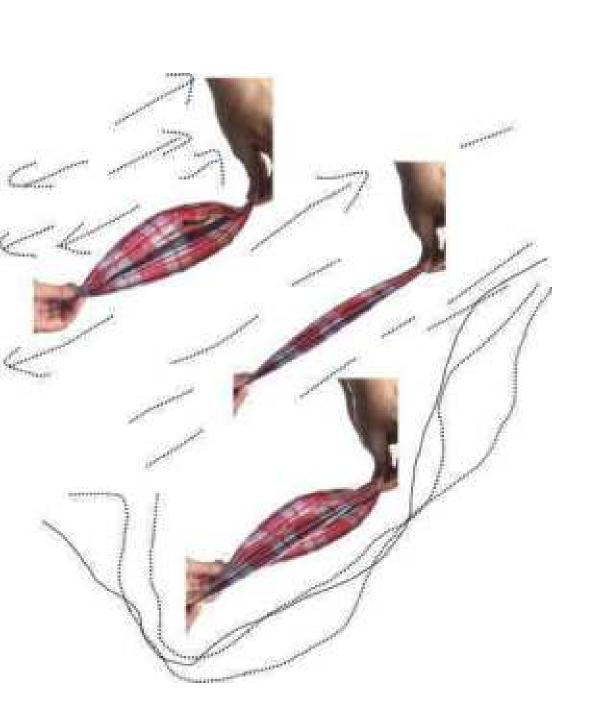

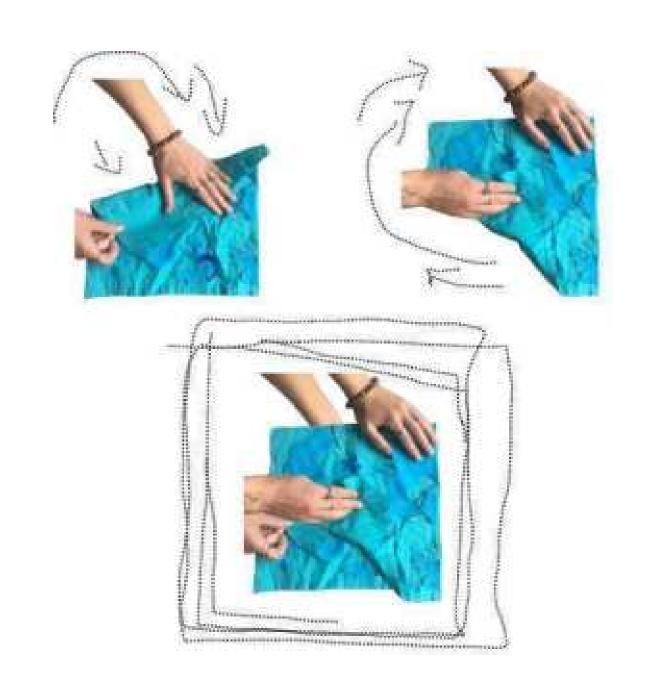

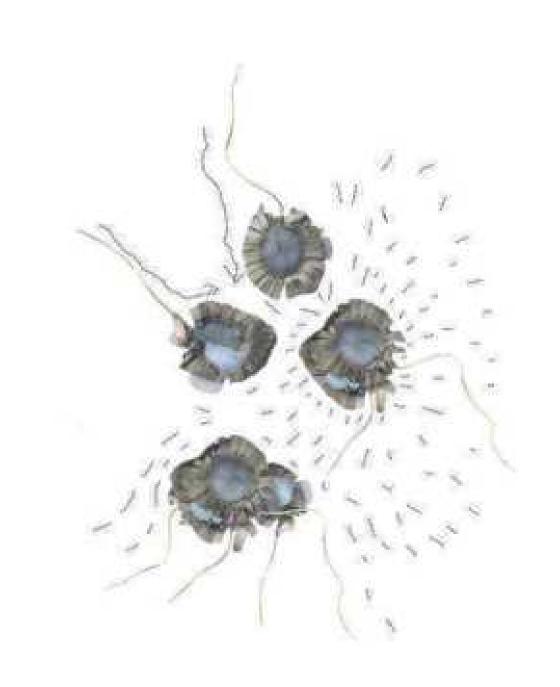



#### DESIGN RESEARCH



Crafted Logic / Ebru Kurbak & Irene Posch

#### DESIGN RESEARCH





Embroidered Computer / Ebru Kurbak & Irene Posch


### FASHION



Solar Shirt / Pauline van Dongen


### FASHION



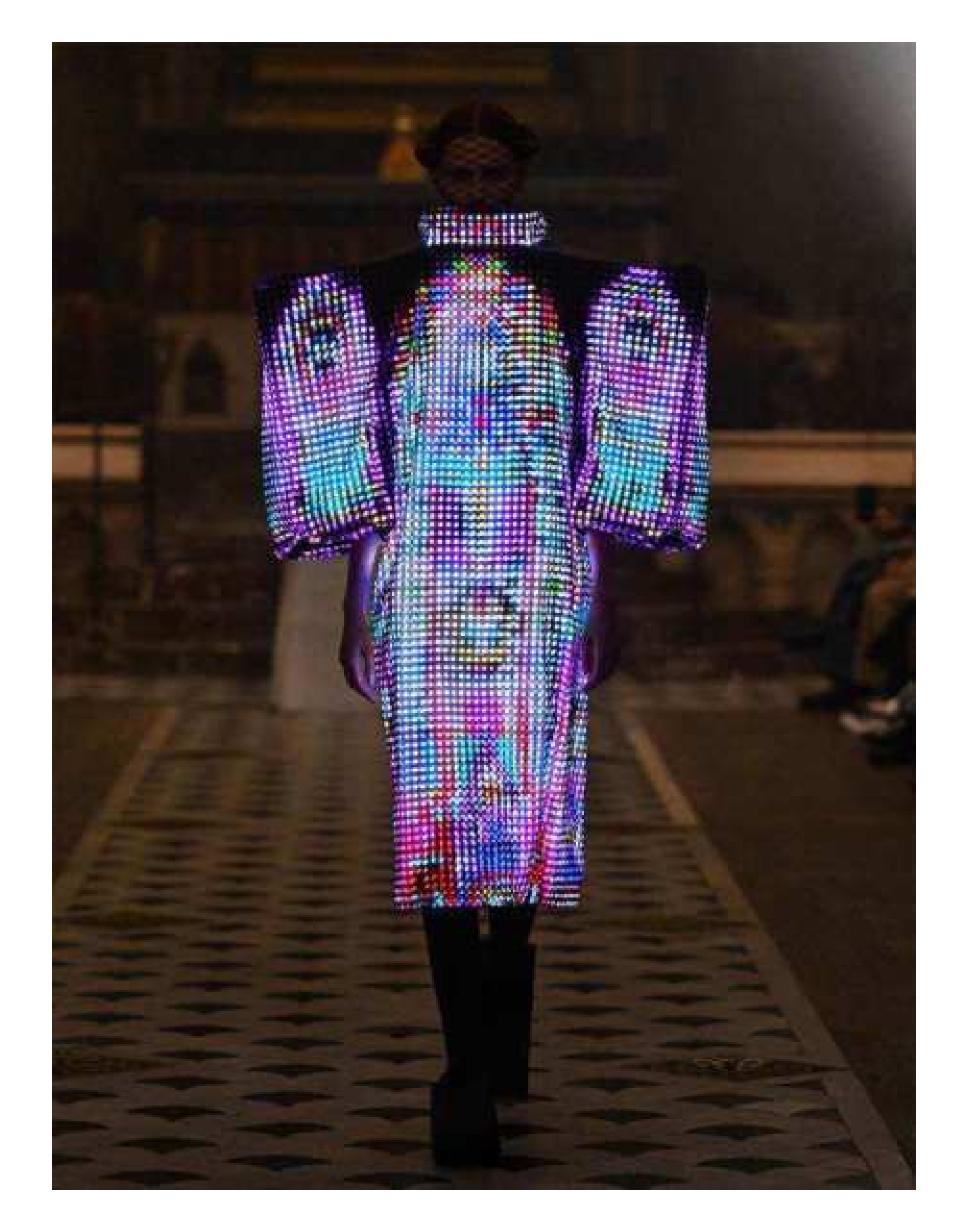



Kunihiko Morinaga for Anrealage / Fall 2025

#### ART

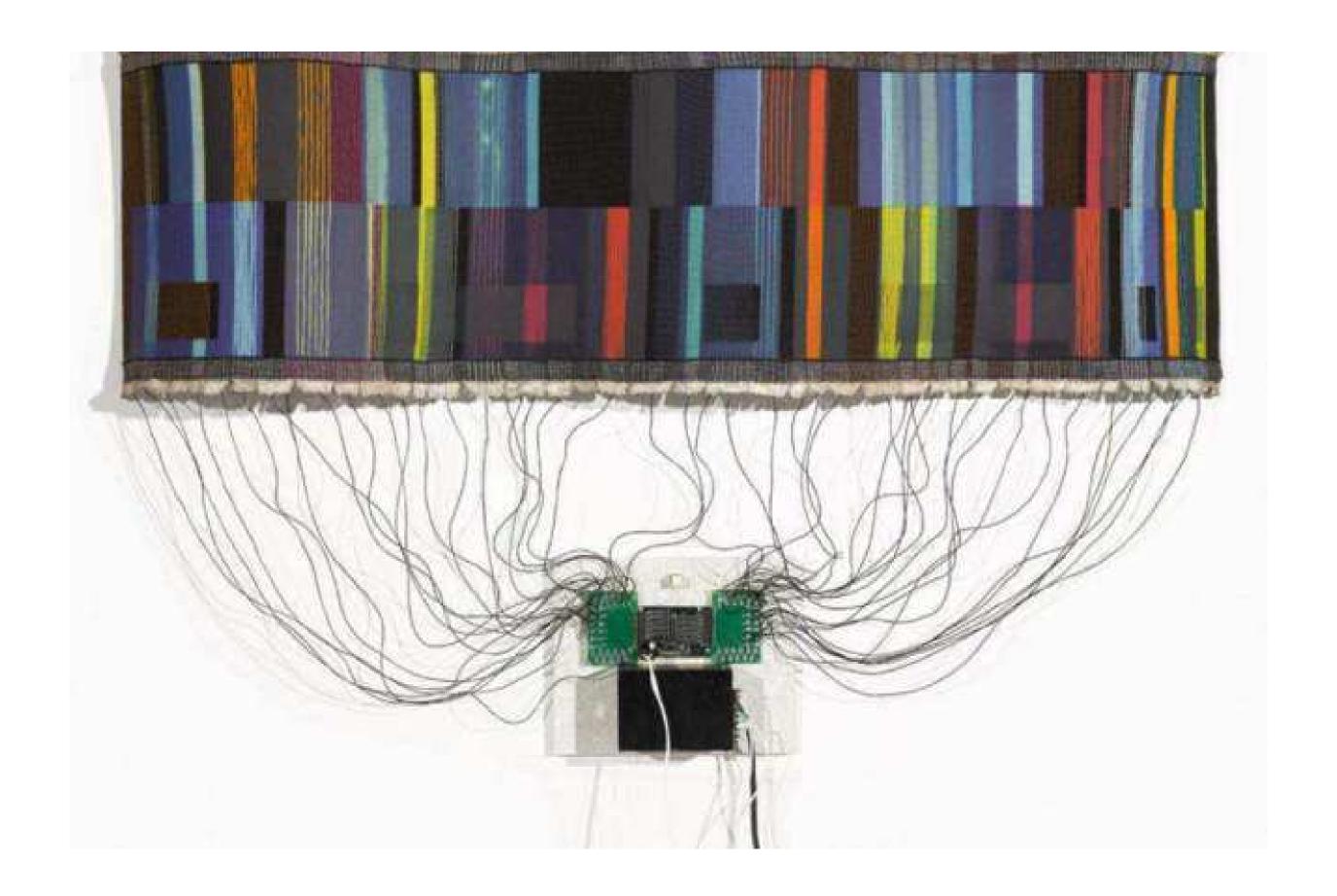


#### ART

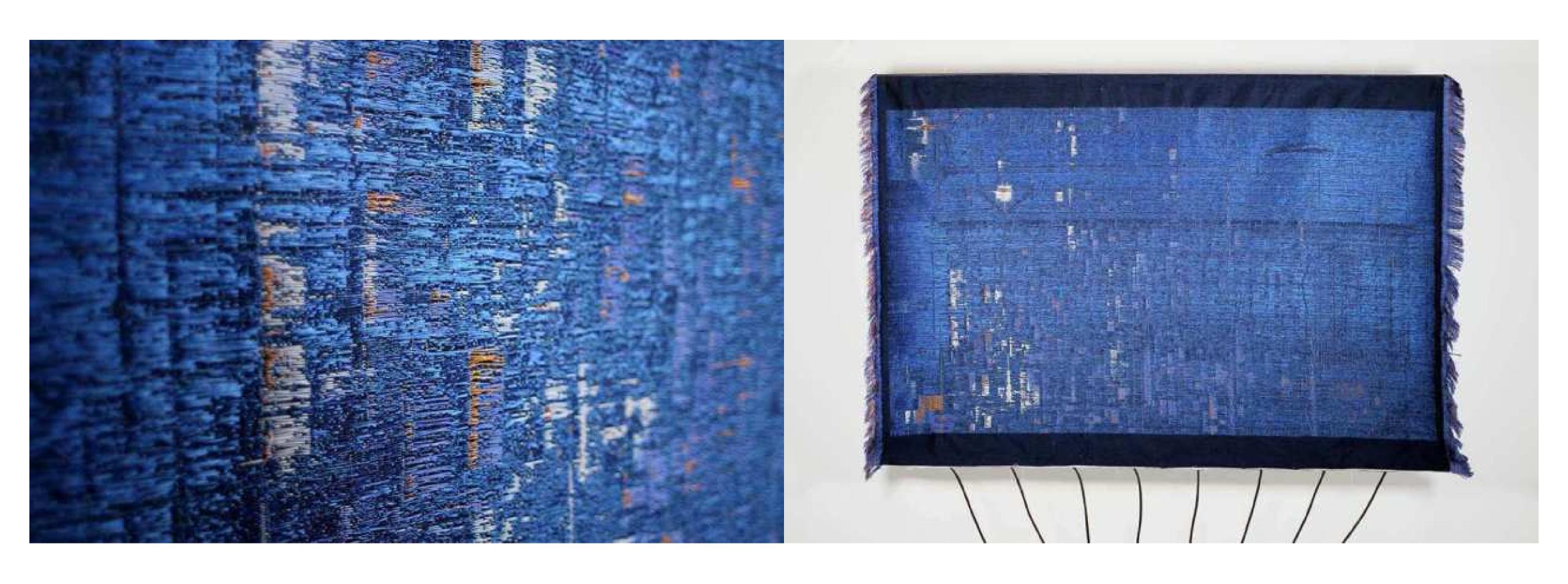

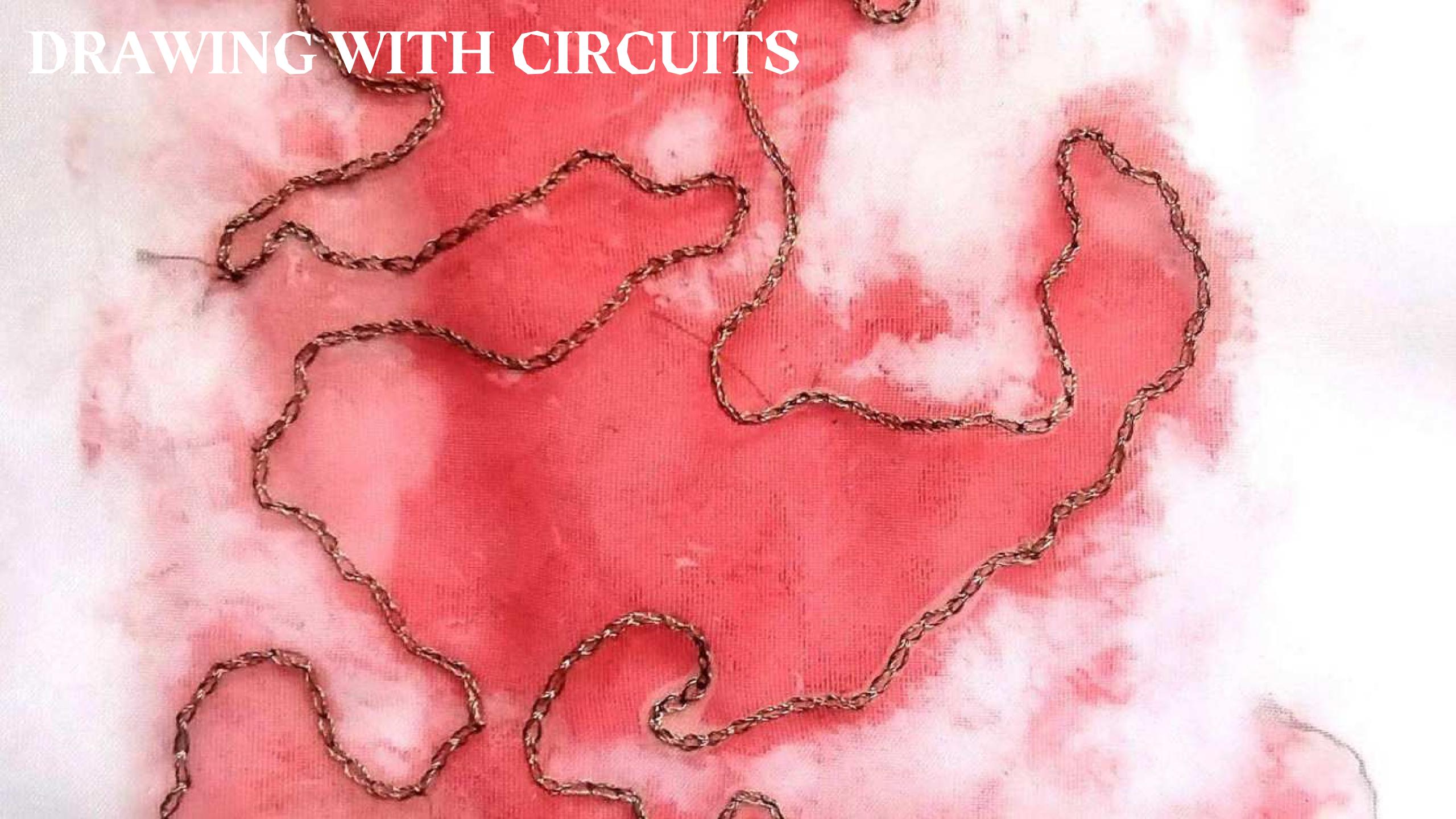


# ELECTRONICS 101

explained using pop songs -

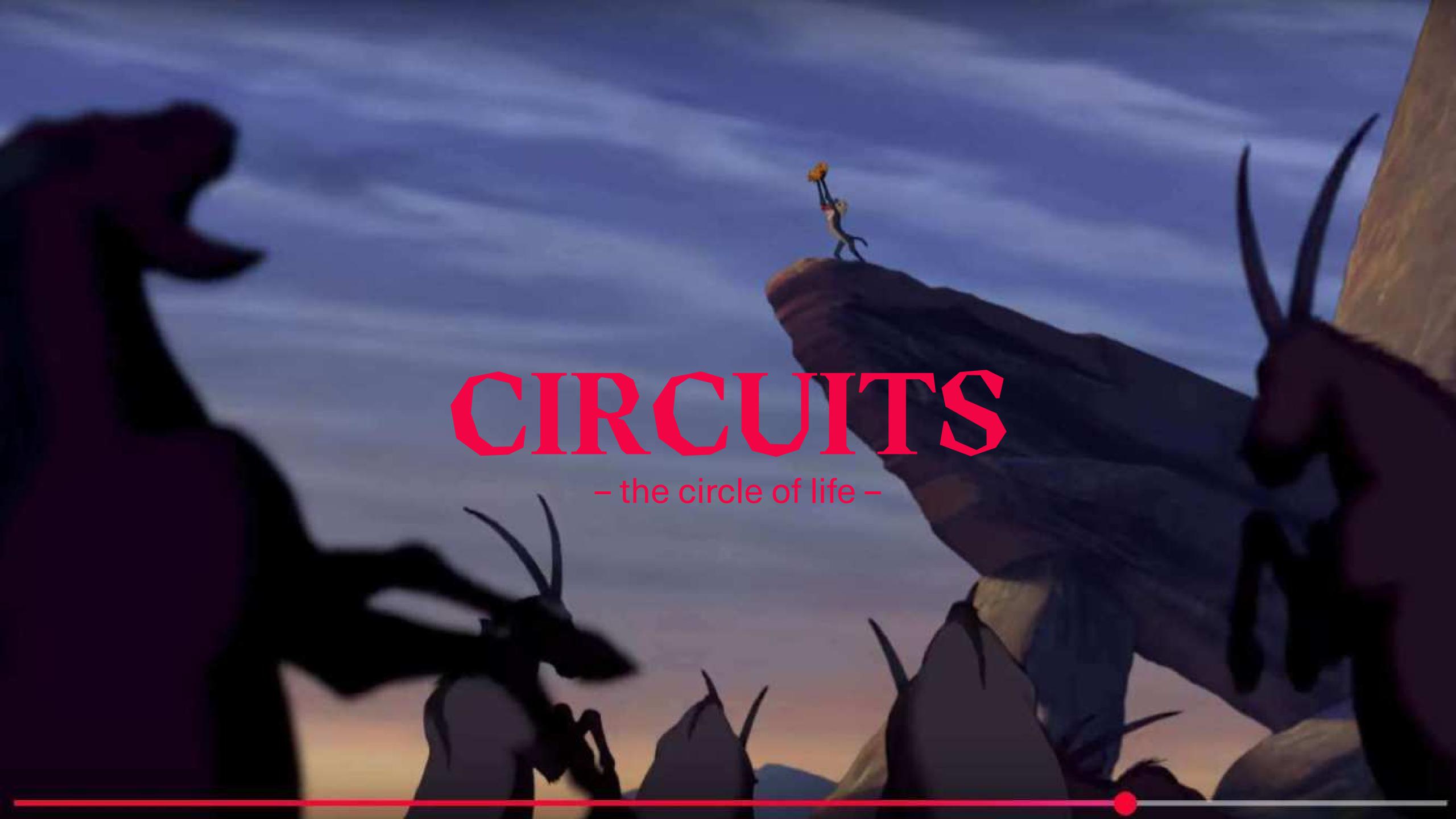
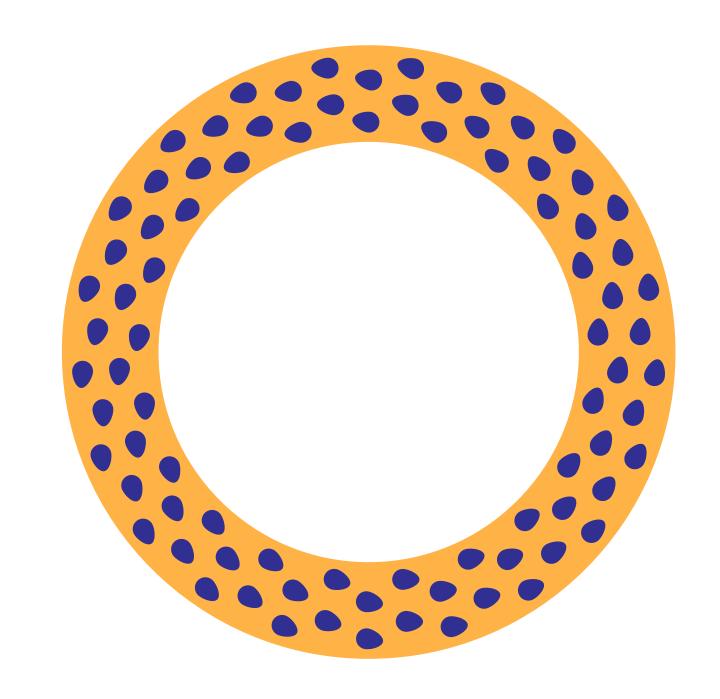
#### AN ELECTRICAL CIRCUIT


A closed conductive loop that features some electrical components, like a power source and a load.



#### CONDUCTIVE MATERIALS






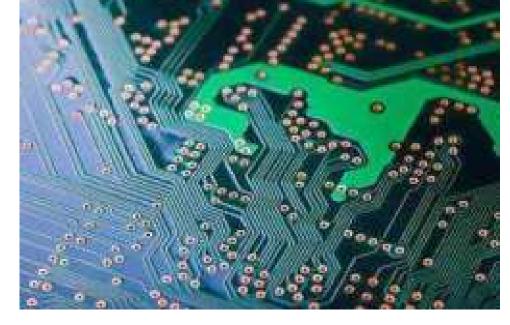






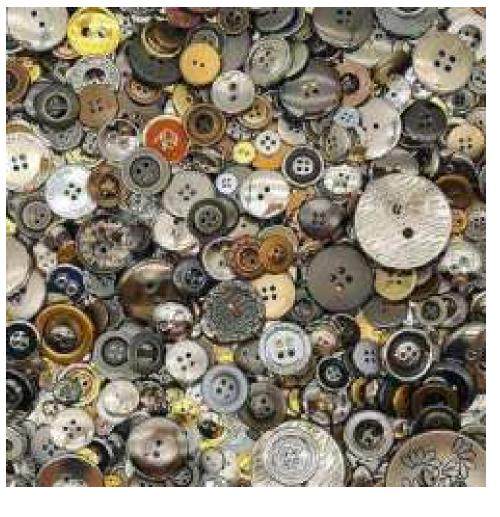







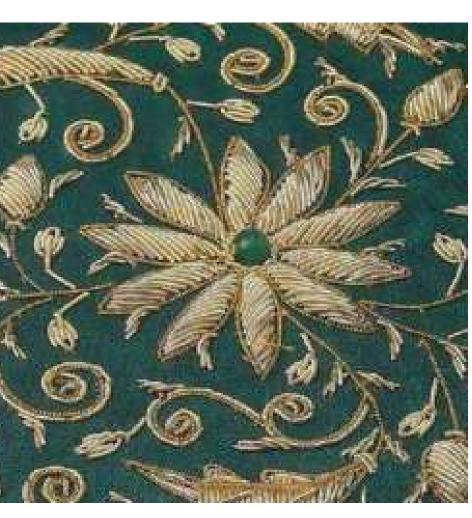


#### CURRENT

Property of a Circuit

~ how much electrical charge is moving through the circuit?


Unit: Ampère (A)

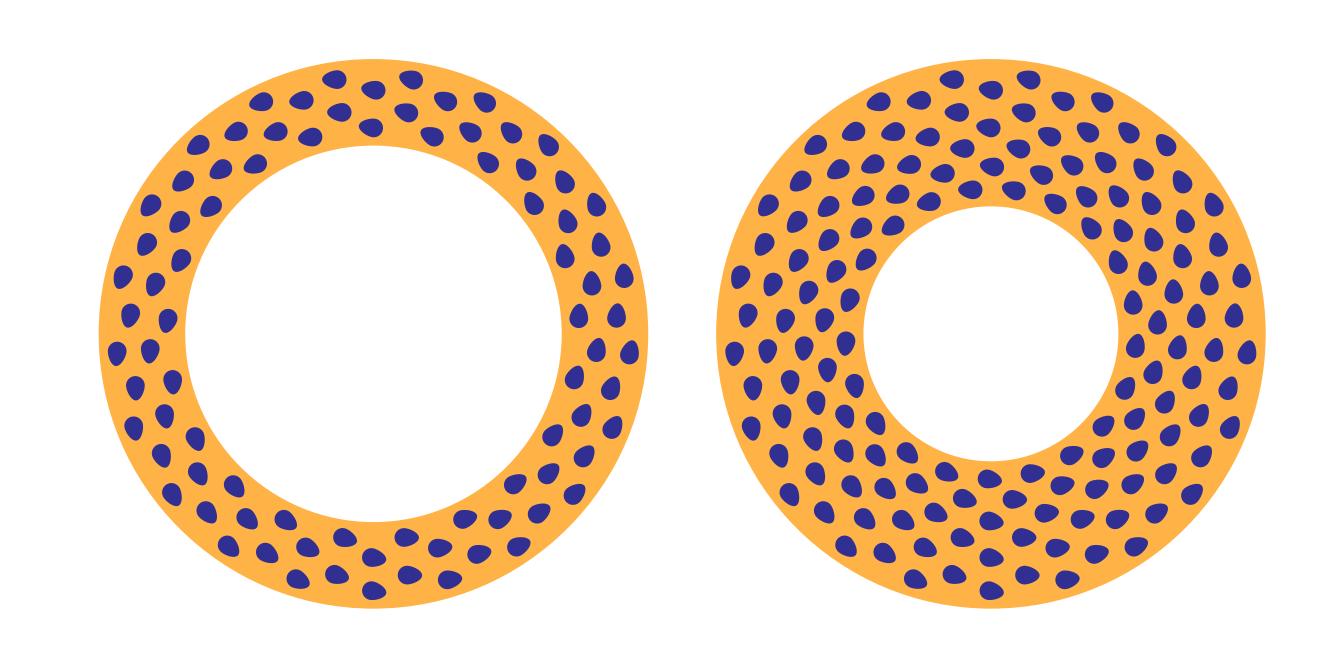


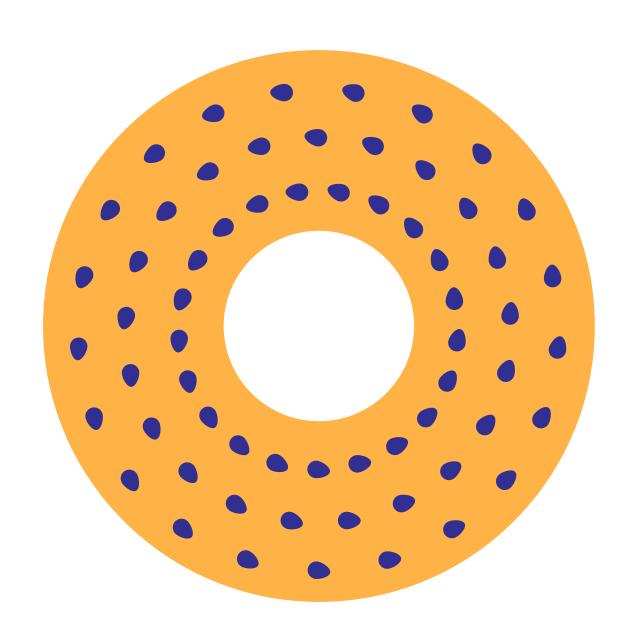
#### **VOLTAGE**

Property of a Circuit
~ motivation for the electrical
charge to move
Unit: Volt (V)
Electrical components are usually
rated a a certain voltage.





less motivation to move




high motivation to move
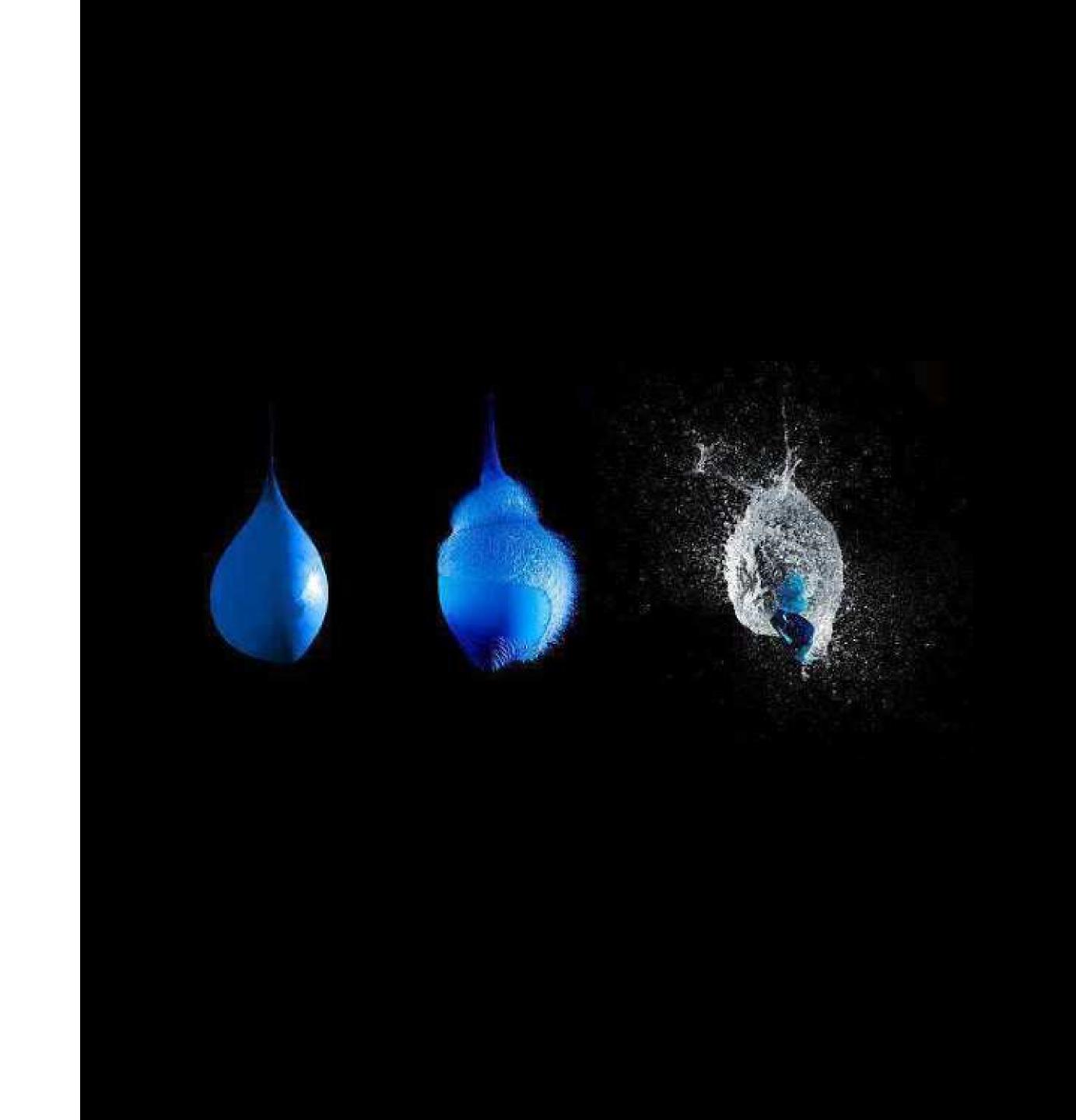
## QUEENINTERLUDE

- under pressure -

voltage ~ pressure difference: particles move to equalize pressure differences



#### RECAP

A functional circuit needs to be closed.

Current (Ampère): How much is moving?





Voltage (Volt):
How high is the motivation to move?







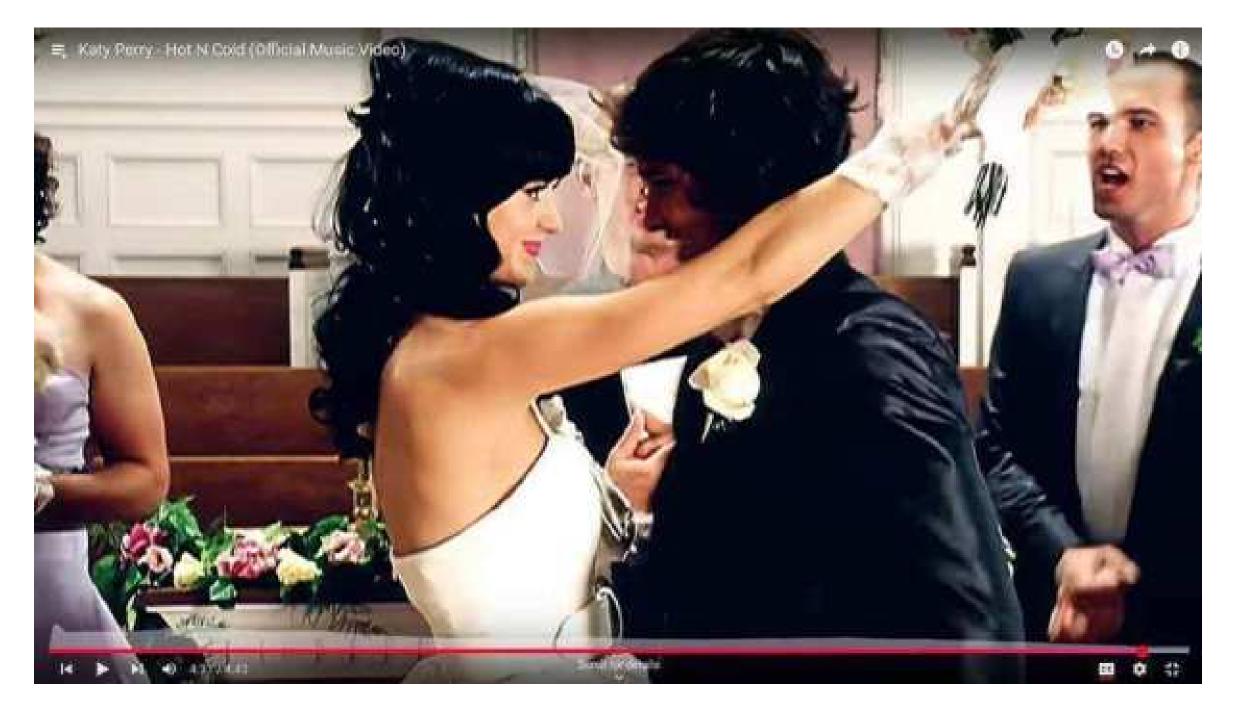
#### SWITCH

A component to open and close the circuit in a controlled way.








Fullfill societal expectations:
get married, have kids.
-> current is flowing, components
can perform as expected

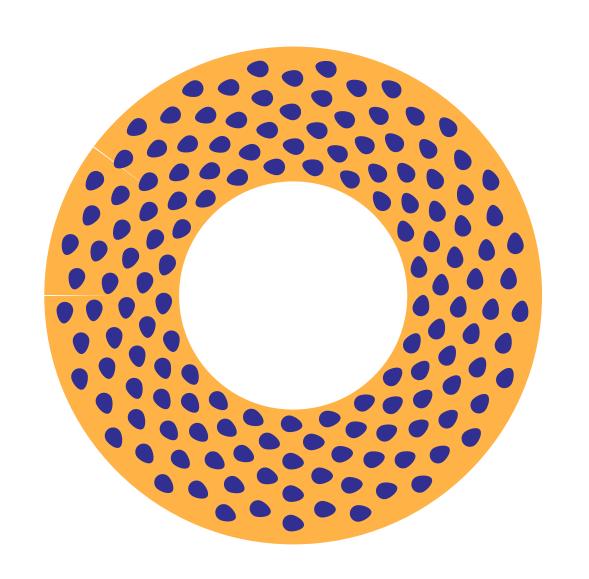
Run away:
find happiness elsewhere.
-> no current is flowing,
components are not functional







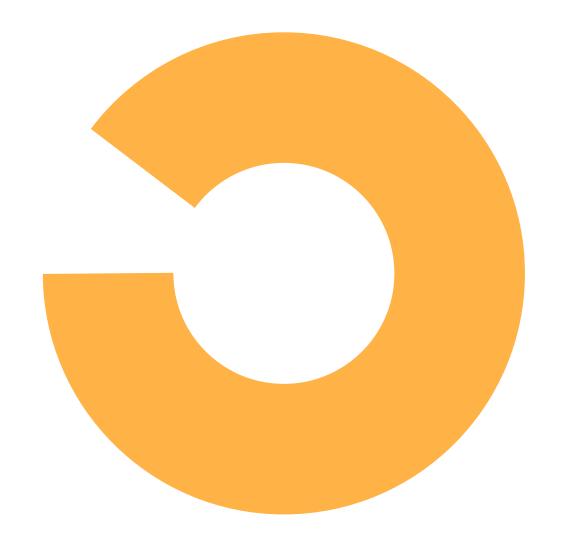Once the circuit is broken, no current will flow anywhere -> it doesn't matter where the switch is placed



# SOFT SWITCHES

Kobakant




Toggle Switch - Liza Stark



Tilt Switch - Kobakant



Neoprene Switch - Kobakant

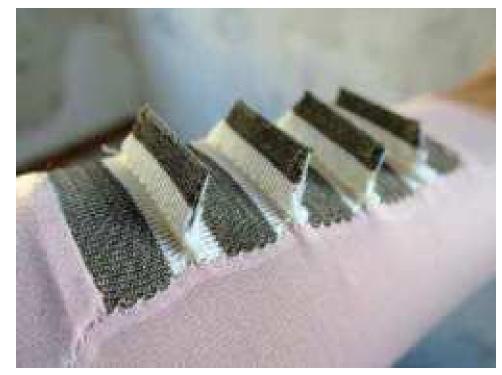

Stroke Switch - Kobakant



Stroke Switch - Liza Stark



Sliding Danish Crown Switch - Kobakant



Push Button - Kobakant



Velcro Switch



**Button Switch** 





#### POWER SUPPLY

A component that provides energy for the circuit.

Usually rated with:

- voltage
- maximum current





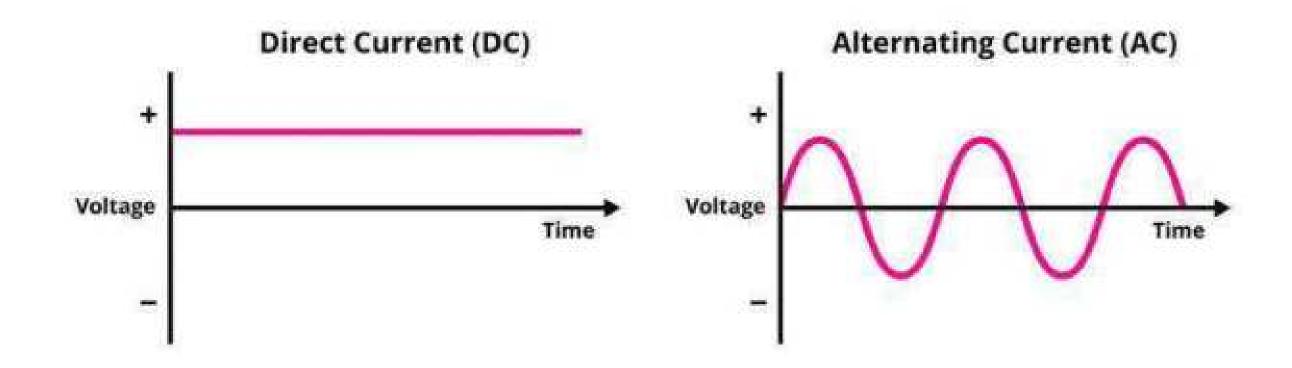
#### AC vs DC

Direct Current:
More for senstitive electronics
& storage

Alternating Current:
Used for electric grids & heavy
machinery





~ DC: Angus performs the "duckwalk" in same direction



~ AC: Angus keeps switching directions

### WHAT'S IMPORTANT:

We will use DC current at max 5V.

-> safe to handle and touch

Still:

Careful with short circuits (\*\*)

# POWER SOURCES / SUPPLIES









Disposable Vape Batteries



Heliatex – Flexible Solar Panels





Automatic Watch – Hand movements of wearer are used to generate power



Grandfather clock using gravity as power source



Suntex – Pauline van Dongen – Woven Solar Panels



Computational Compost –

Marina Ottero – Using compost as a power source for datacenters





#### RESISTORS

A component that limits the amount of current in a circuit.


Important because:
No resistance -> unlimited
current -> short circuit




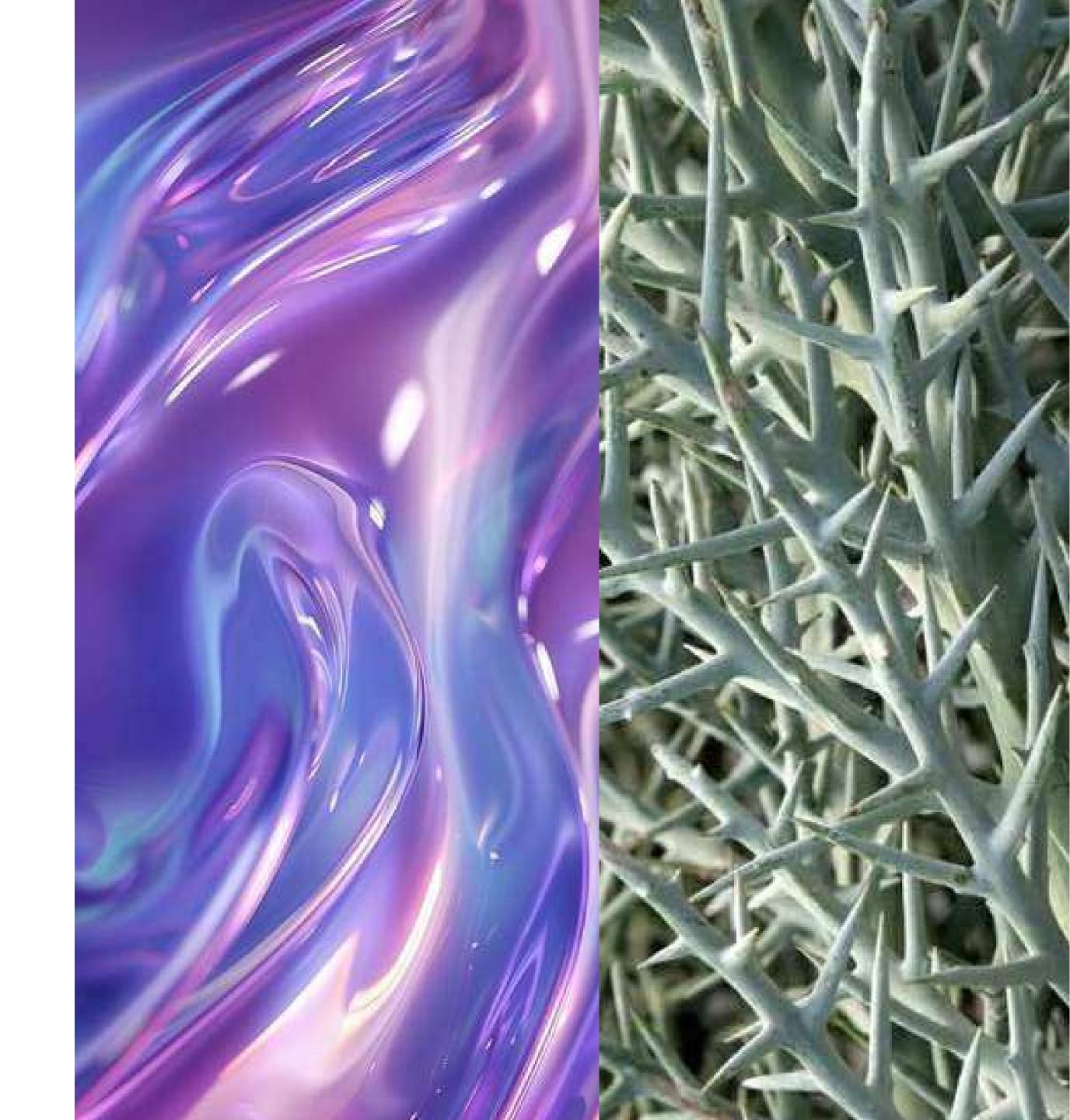
### RESISTANCE

Property of materials  $\sim$  How well does current pass through? Unit:  $\Omega$  (ohm)



#### THREADED RESISTANCE

The resistance of conductive thread depends on several factors:

- blend of fibres
  - tension
  - -> technique













# EXCESS HEAT


the electrical energy dissipates as heat

~ things getting hot from friction.




The total resistance limits the current in the ~whole circuit

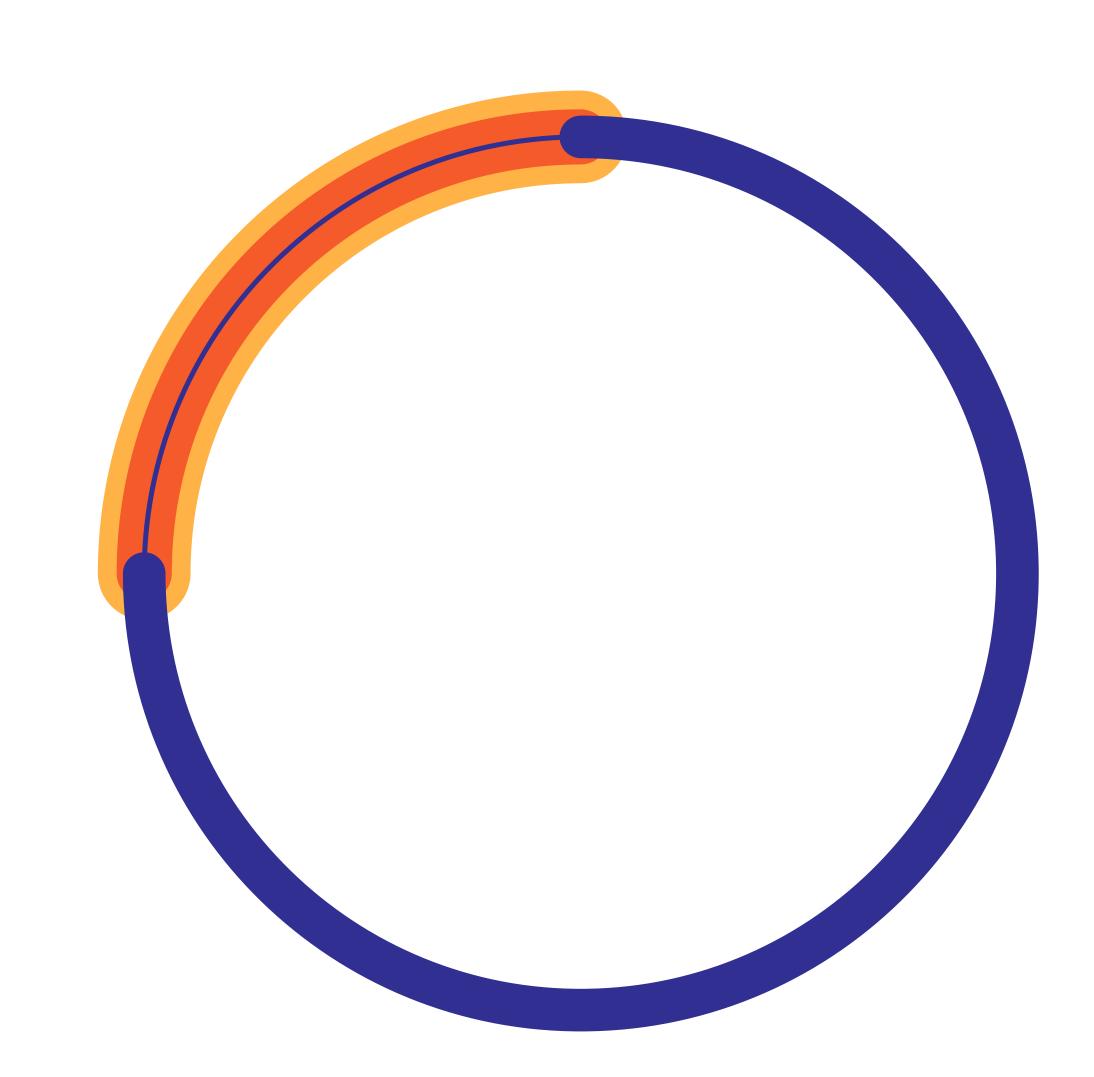-> heat dissipates where the resistance is high.



# LET'S GET PRACTICAL!

# THERMOCHROMATIC INK

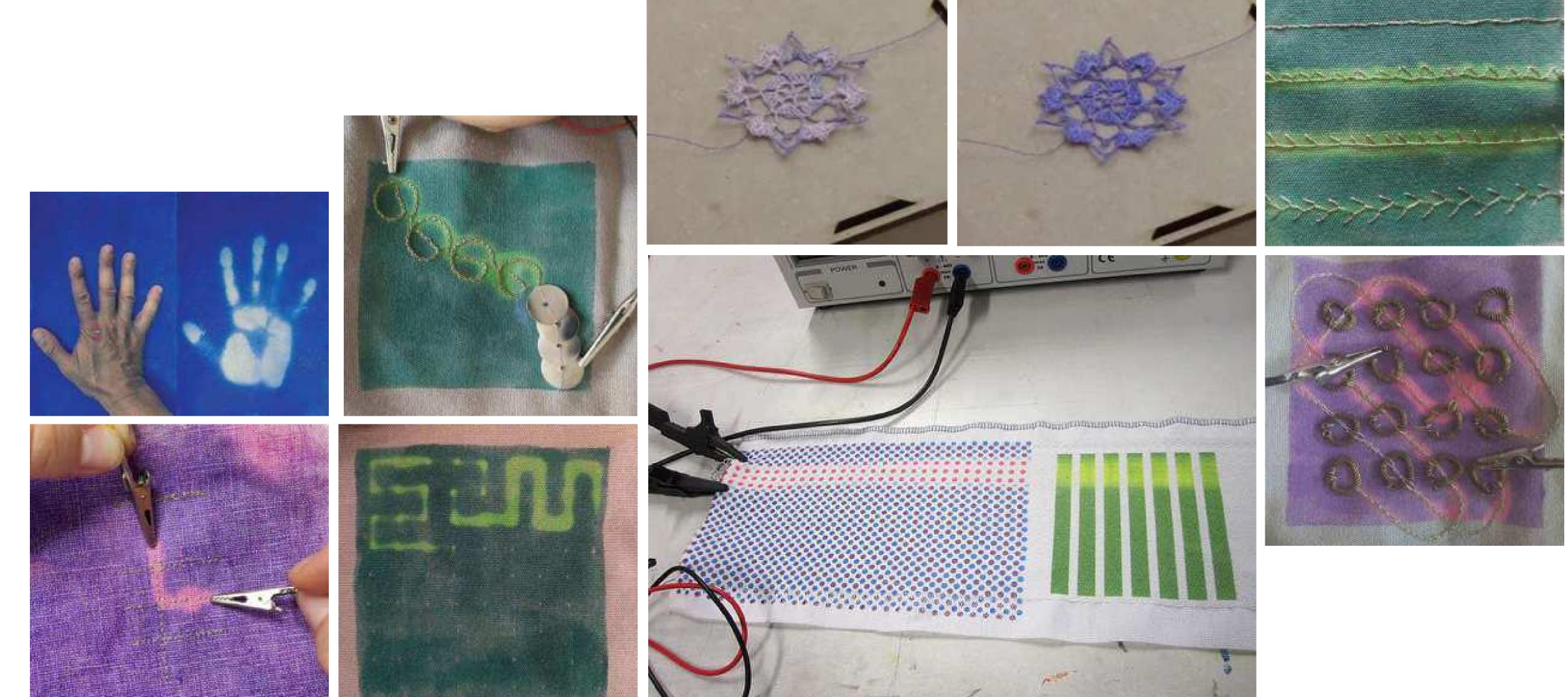







# THE POUCH




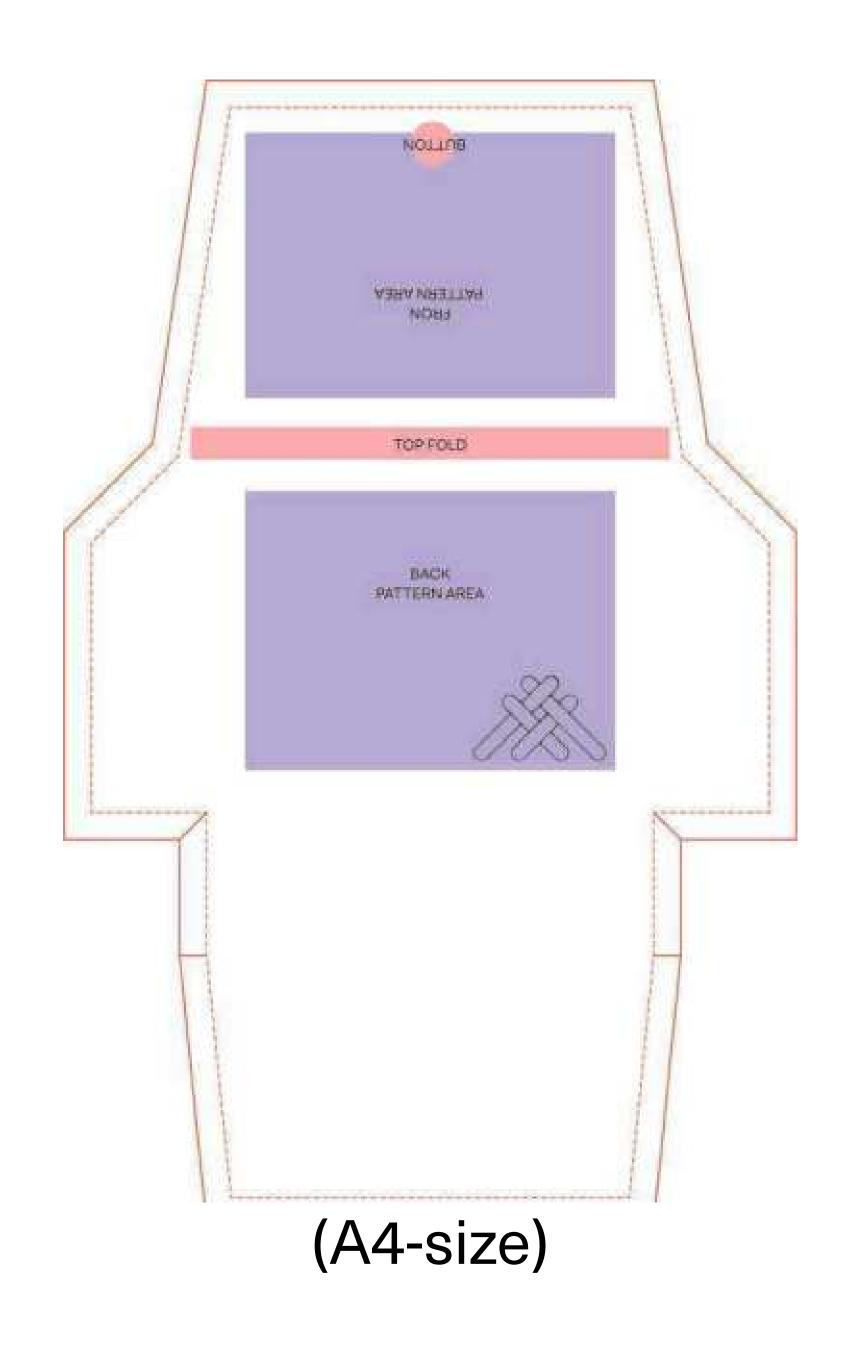

## THE CIRCUIT

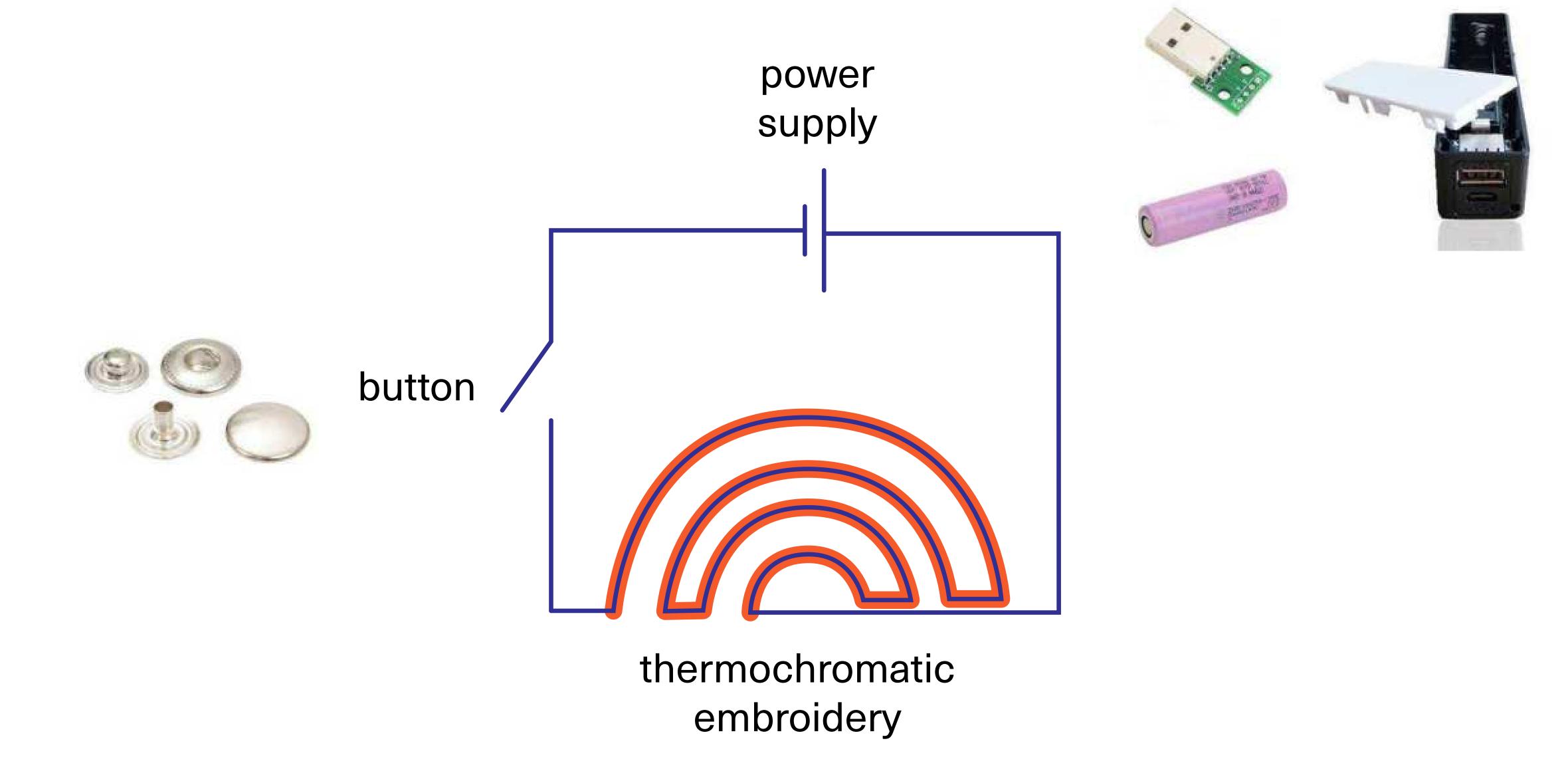

# PATTERN EXAMPLES

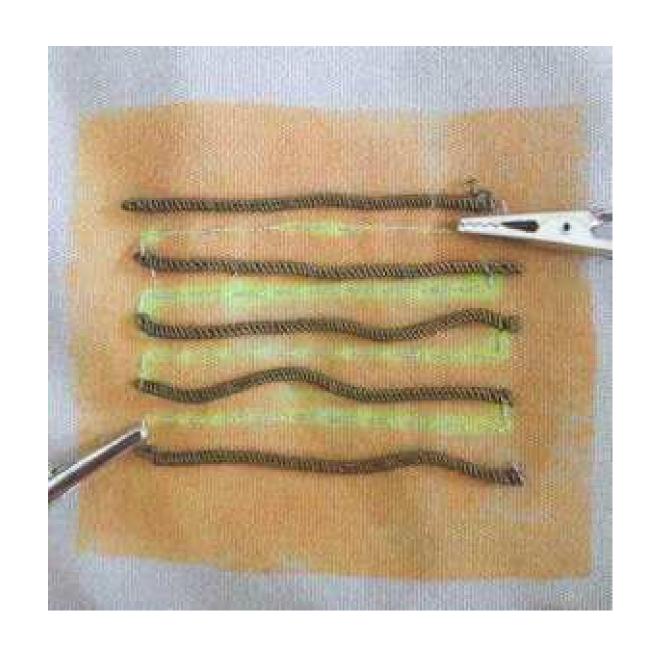










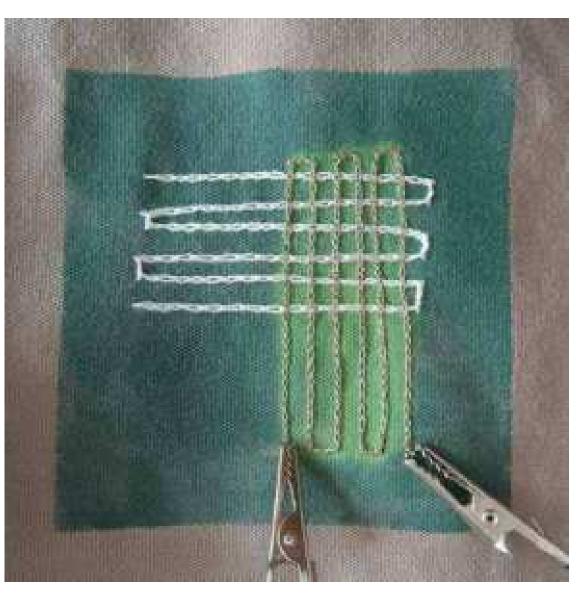

#### DESIGNING THE CIRCUIT

Basic requirements:

a closed circuit between the + and - of the battery.

a total resistance that's higher than 5  $\Omega$  (otherwise  $\ensuremath{\ensurema$ 

a total resistance that's lower than ~85  $\Omega$ 

#### HOW TO MEASURE RESISTANCE

- 1. Set the multimeter on the  $\Omega$  symbol
- 2. Touch the beginning and end of the resistor you would like to measure



#### THE SET-UP

Create an embroidered pouch with a color-changing design that is revealed when the pouch is closed

- 1. Design a color-changing circuit, using a battery, a button as a switch and conductive thread as a resistor on the pattern of the pouch.
- 2. Embroider it on the thermochromatic fabric with the conductive thread.
- 3. Assemble the pouch!

#### EMBROIDERY STITCHES

Running Stitch

1 thread = 1 R

1 + 2 threads = 1/3 R

**Back Stitch** 

2 + 1 threads = 1/3 R


Chain Stitch


2 + 2 threads = 1/4 R

Whipped Back Stitch

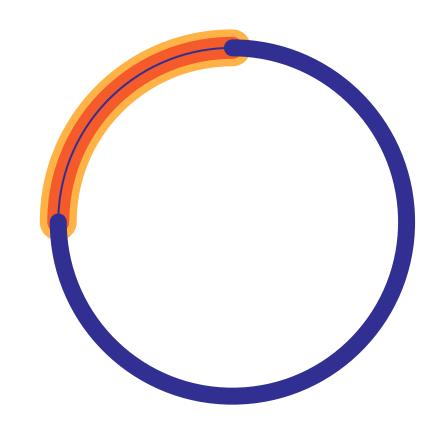
#### DIRECTING THE COLOR CHANGE


if you mix stitches-> more color change around stitches with high resistance



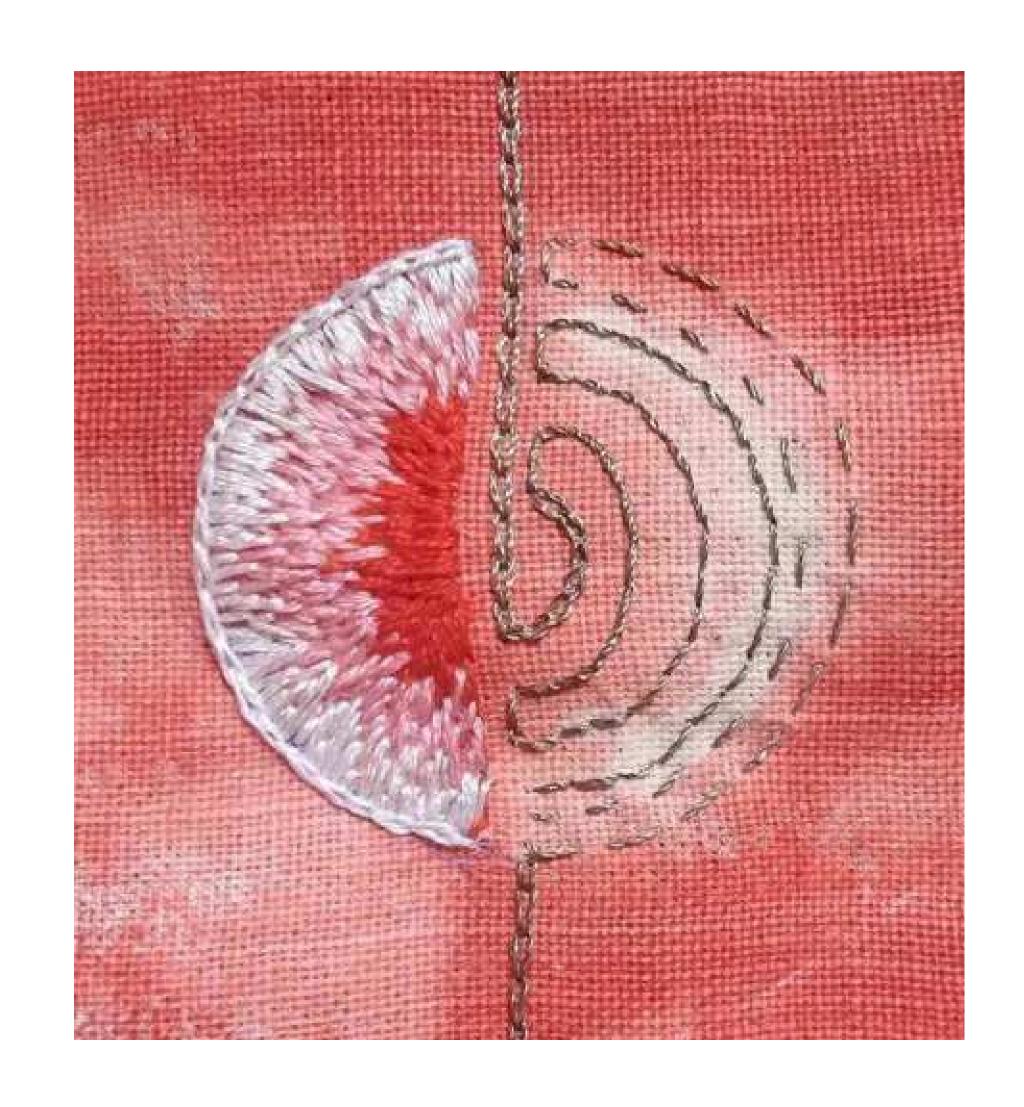


# SERIES VS PARALLEL CIRCUITS

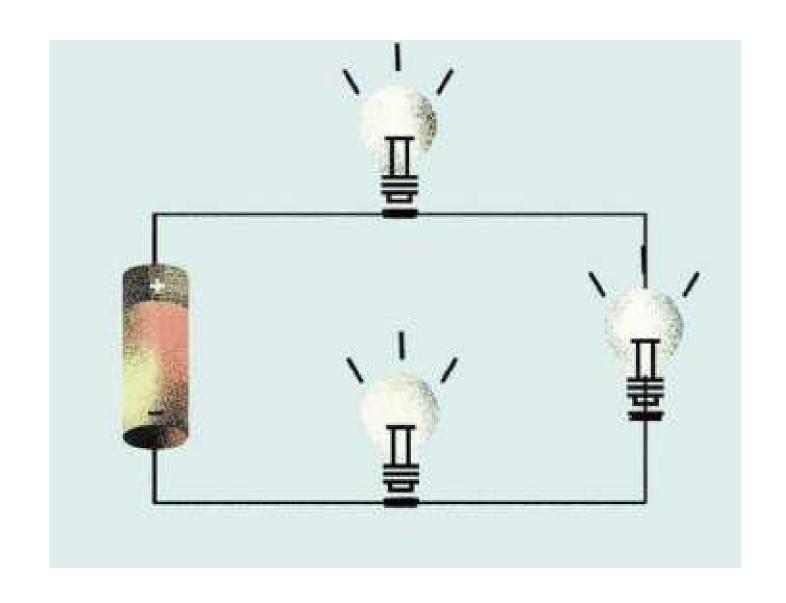

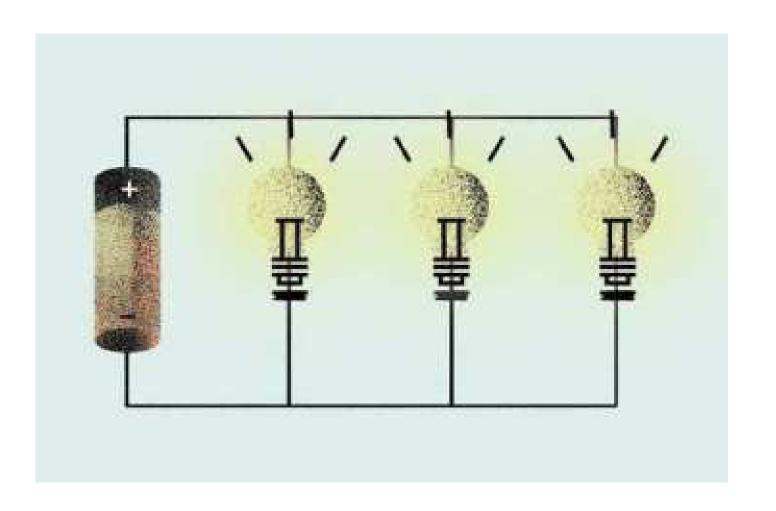
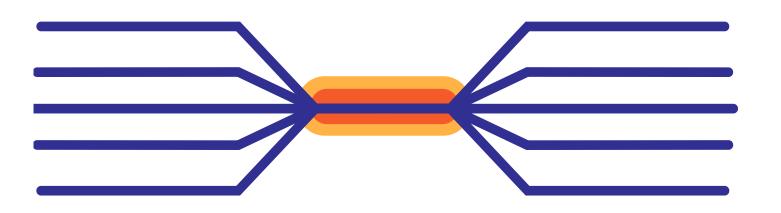
#### PARALLEL CIRCUITS

the current is split among several paths -> less total resistance







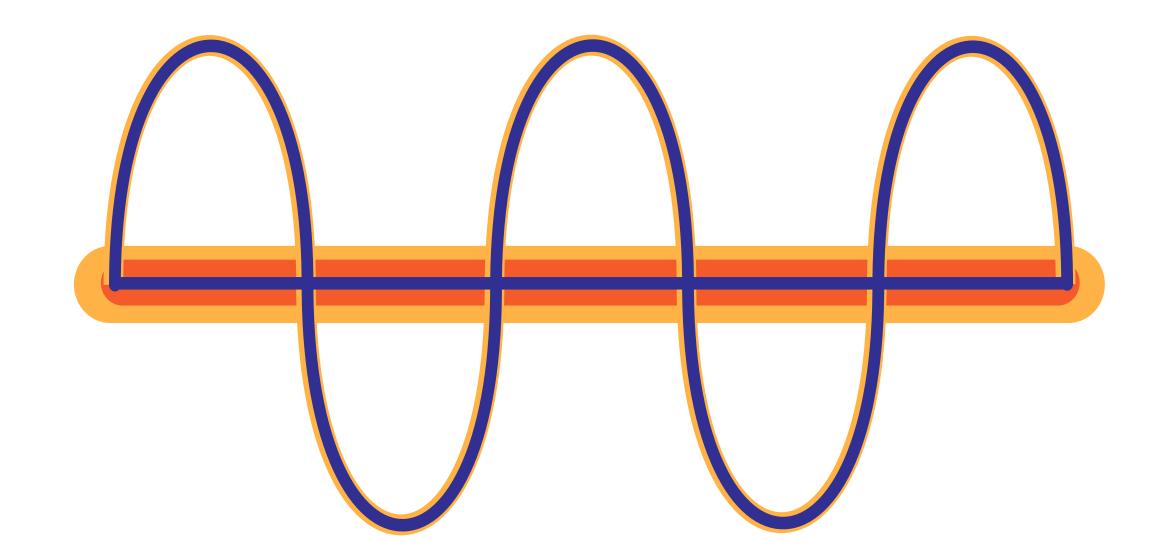
#### PARALLEL CIRCUITS II

the current is split proportionally to the resistance of the individual paths

-> the current will primarily chose the path of least resistance



# THANK YOU & LETS KEEP IN TOUCH!:)



Rebekka Jochem www.rebekkajochem.com reb.jochem@googlemail.com